

## EECE 2306-06 Digital Systems Engineering I

# 2-Digit Seven-Segment Binary Converter

### 1. Project Overview

The purpose of this project is to design and implement a binary-to-decimal converter that displays a 2-digit decimal number (00-99) using two seven-segment displays. The input will be an 8-bit binary number, which will be converted to its decimal equivalent and displayed on the seven-segment displays. The design must be implemented using only combinational logic components such as logic gates, multiplexers, demultiplexers, encoders, and decoders. Microcontrollers and programmable devices are not allowed.

### 2. System Requirements

A functional and complete project must comply with the following requirements:

- The system must accept an 8-bit binary input (0 to 255).
- The system must convert the binary input into its decimal equivalent.
- The system must display the least significant two decimal digits (00-99) on two seven-segment displays.
- The display must be updated in real-time when the binary input changes.
- Combinational logic circuits using logic gates, multiplexers, demultiplexers, encoders, and decoders. No microcontrollers, FPGAs, or any programmable devices may be used.
- Two seven-segment displays (common anode or common cathode).
- Binary input provided using DIP switches or push buttons.
- Power supply (typically 5V for logic circuits and display operation).
- No microcontrollers, FPGAs, or any programmable devices may be used.

Pages

① Introduction

① Definition of Main Concepts

⑦-⑩ Development

①-② Results

① Conclusion

① References

\* No One-Page Photos

\* Single or Double Spaced

\* Times New Roman/Arial 12 Pt Size

\* Navigation: Title, Heading, Heading 2, Heading 3

\* Save-as PDF

draw.io